


Ian Fritz Dual T/G/T/S/H

Threshold/Gate/Trigger/Sample/Hold Circuit

This is a circuit that combines two important synthesizer functions. It produces trigger and gate signals whenever a "timing" signal input crosses a user-defined threshold. At the same time, the trigger pulse fires a high-performance sample-and-hold circuit that samples a second "main" signal input. Two of these circuits are contained on a single board..

The Random*Source CHAQUO + TGTSH kit contains a main pcb for the TGTSH (comprising two identical circuits) and a matching component pcb serving as an interface to the front panel.

Main pcb:

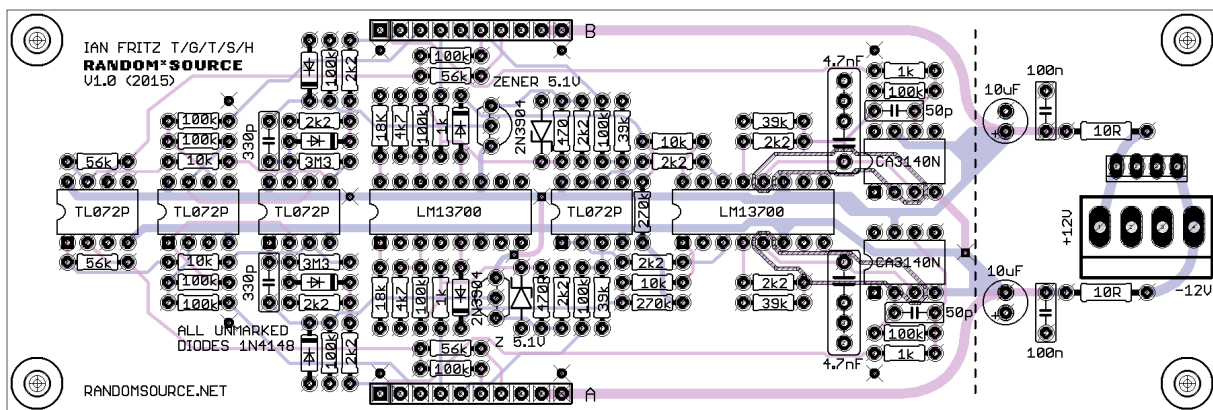

Please note:

- With the recommended IC's this circuit has a very small droop rate of under 2 mV/sec and can sample at rates up to over 10 kHz. The CA3140 mosfet-input buffers can be replaced with low input-bias opamps. With OPA134's, the droop rate is increased to ~12 mV/sec. Expensive opamps with input bias currents under 10 pA make satisfactory substitutes, but at present the CA3140 is still in production and only costs around \$1.
- Pcb contains 2 ring guards - be careful when soldering the relevant pins of the CA3140s and the LM13700.
- Assembly of the Random*Source module is described in the CHAQUO documentation.
- Orientation of the main pcb: **power header is at the bottom** (when looking at the module up-right, e.g. in a rack).
- Module is designed to be powered by a +/-12V stabilized PSU, +/-15 V should work fine also.

Bill of Materials

Resistors (1%)

2	10R	F1, F2	alt: ferrit beads
4	1k	A-R15, B-R15, B-R27, R27	
10	2k2	A-R11, A-R13, A-R14, A-R22, A-R24, B-R11, B-R13, B-R14, B-R22, B-R24	
2	4k7	B-R17, R17	
4	10k	A-R7, A-R23, B-R7, B-R23	
2	18k	B-R18, R18	
4	39k	A-R21, A-R25, B-R21, B-R25	
4	56k	A-R4, A-R6, B-R4, B-R6	
14	100k	A-R2, A-R5, A-R8, A-R10, A-R20, B-R2, B-R5, B-R8, B-R10, B-R16, B-R20, B-R26, R16, R26	
2	270k	A-R19, B-R19	
2	3M3	A-R9, B-R9	

Capacitors

2	50p or 47p	B-C3, C3X	COG/NPO 10% or better
2	330p	A-C1, B-C1	COG/NPO 10% or better
2	4.7nF	A-C2, B-C2X	Styrene (10% or better)
2	100n	C3, C4	Bypass caps
2	10uF	C1, C2	Electrolytic

ICs

6	1N4148	A-D1 , A-D2, A-D4, B-D1, B-D2, B-D4	1N4148 (or similar) switching diode
2	CA3140N	U7-A, U7-B	(or other low bias-current opamp)
2	LM13700	U4, U6	OTA
4	TL072P	A-U1, A-U2, U3, U5	or similar op amp
2	ZENER 5.1 V	A-D3 , B-D3	5.1 V Zener diode
2	2N3904	A-T1, B-T2	NPN Transistor

Misc

4	Potentionmeter 100k	linear (B100K)	Alpha 9mm vertical pcb mount available from Thonk, Tayda
1	MTA-156		MTA-156 power connector
2	SIL header 10pol		8-pin connector, links main pcb to component pcb
8	Banana Jacks		Emerson-Johnson Thonk / Mouser: 530-108-0903-1 (black)
4	Potentionmeter 50k or 100k	linear (B50K or B100K)	Alpha 9mm vertical pcb mount available from Thonk, Tayda


Building and Module Assembly

The module shares a component pcb with the Ian Fritz CHAQUO - **please refer to the Random*Source CHAQUO documentation** for the assembly of the module.

Setup and Operation

There are no calibration or other adjustments for these circuits.

Original Schematics

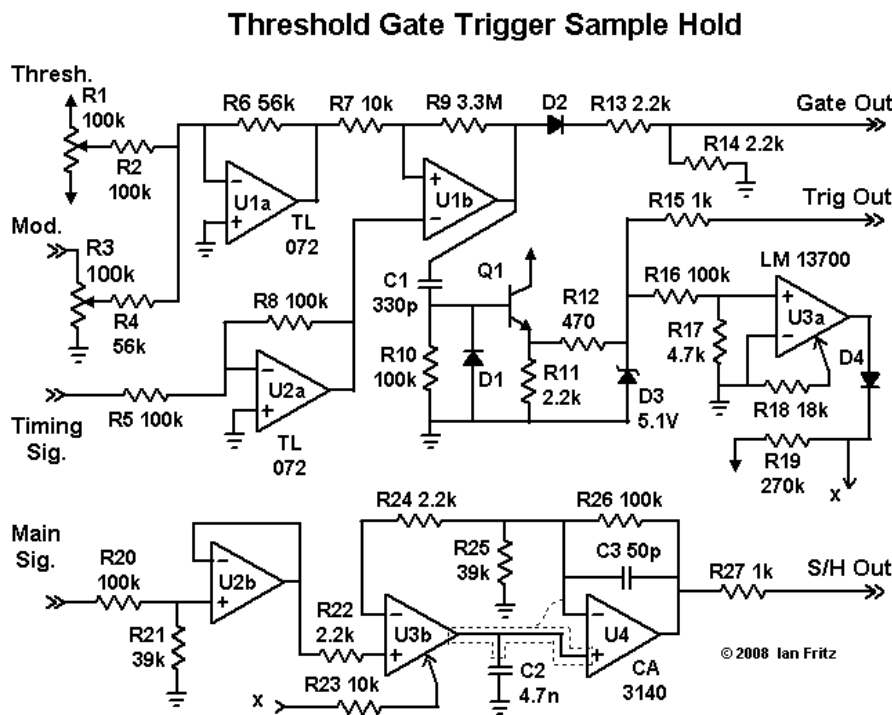

(Version 01 February 2017)

Text in italics is from the original documentation by Ian Fritz. Module and circuit under license from Ian Fritz. All rights reserved.